

## 第二次實驗報告

題目：

**Time-of-day clock**

姓名：黃子軒

**學號：310581003**

繳交日期：111 年 10 月 24 日

## 1. 實驗目的

透過本次實驗，除了熟悉如何撰寫 verilog 並實現於 FPGA 板，更學習一些常見 Sequential circuits (latches, flip-flops, registers) 與 Counters 的架構及運作原理，並嘗試結合其電路實現一個具有小時、分鐘、秒的計時時鐘。

## 2. 實驗程式碼

```
module Lab2_part7(CLOCK_50, HEX0, HEX1, HEX2, HEX3
                  , HEX4, HEX5, SW[9:0]);

    input CLOCK_50;

    input [9:0]SW;

    output [6:0]HEX0;

    output [6:0]HEX1;

    output [6:0]HEX2;

    output [6:0]HEX3;

    output [6:0]HEX4;

    output [6:0]HEX5;

    wire clock_out;

    wire [3:0] Q0;

    wire [3:0] Q1;

    wire [3:0] Q2;

    wire [3:0] Q3;

    wire [3:0] Q4;

    wire [3:0] Q5;

    div clock_div(clock_out, CLOCK_50);

    counter0 CTR0(clock_out, carry01, Q0, Q1);

    seven_segments s0(clock_out, Q0, HEX0);

    seven_segments s1(clock_out, Q1, HEX1);
```

```

counter1 CTR1(clock_out, carry01, SW[8], SW[9], SW[7:0], carry12, Q2, Q3);

seven_segment s2(clock_out, Q2, HEX2,SW[8]);

seven_segment s3(clock_out, Q3, HEX3,SW[8]);


counter2 CTR2(clock_out, carry01, SW[8], SW[9], SW[7:0], carry12, Q4, Q5);

seven_segment s4(clock_out, Q4, HEX4,SW[8]);

seven_segment s5(clock_out, Q5, HEX5,SW[8]);

endmodule

```

// Second //

```

module counter0(Clk, carry01, Q0, Q1);

    input Clk;

    output reg carry01;

    output reg [3:0] Q0;

    output reg [3:0] Q1;

    always @(posedge Clk)
    begin
        if (Q0==4'd9 & Q1!=4'd5)
            begin
                Q0<=0;

                Q1<=Q1+1;

                carry01<=0;

            end

        else if (Q0==4'd8& Q1!=4'd5)
            begin

```

```

        Q0<=Q0+1;

        carry01<=0;

        end

    else if (Q0==4'd9 & Q1==4'd5)

        begin

            Q0<=0;

            Q1<=0;

            carry01<=1;

            end

    else if (Q0==4'd8 & Q1==4'd5)

        begin

            Q0<=Q0+1;

            carry01<=0;

            end

    else

        begin

            Q0<=Q0+1;

            carry01<=0;

            end

    end

endmodule

// Minute //

module counter1(Clk, carry01, set, select, SW[7:0], carry12, Q2, Q3);

    input Clk, carry01, set, select;

    input [7:0]SW;

```

```

reg en;

output reg carry12;

output reg [3:0] Q2;

output reg [3:0] Q3;


always @(posedge set or posedge carry01)

begin

    if (carry01==1)

        en<=0;

    else if (set==1)

        en<=1&~select;

    else

        en<=0;

end


always @(posedge Clk)

begin

if(set)

begin

    if (Q2==4'd9 & Q3!=4'd5 & carry01==1)

        begin

            Q2<=0;

            Q3<=Q3+1;

            carry12<=0;

            end

        else if (Q2==4'd8& Q3!=4'd5 & carry01==1)

```

```

begin

Q2<=Q2+1;

carry12<=0;

end

else if (Q2==4'd9 & Q3==4'd5 & carry01==1)

begin

Q2<=0;

Q3<=0;

carry12<=0;

end

else if (Q2==4'd9 & Q3==4'd5 & carry01==0)

begin

carry12<=1;

end

else if (Q2==4'd8 & Q3==4'd5)

begin

Q2<=Q2+1;

carry12<=0;

end

else if (carry01==1)

begin

Q2<=Q2+1;

carry12<=0;

end

else if(en==1)

begin

```

```

        Q2<=SW[3:0];

        Q3<=SW[7:4];

    end

end

else

begin

    if (Q2==4'd9 & Q3!=4'd5 & carry01==1)

        begin

            Q2<=0;

            Q3<=Q3+1;

            carry12<=0;

        end

    else if (Q2==4'd8 & Q3!=4'd5 & carry01==1)

        begin

            Q2<=Q2+1;

            carry12<=0;

        end

    else if (Q2==4'd9 & Q3==4'd5 & carry01==1)

        begin

            Q2<=0;

            Q3<=0;

            carry12<=0;

        end

    else if (Q2==4'd9 & Q3==4'd5 & carry01==0)

        begin

            carry12<=1;

```

```

        end

    else if (Q2==4'd8 & Q3==4'd5)

        begin

            Q2<=Q2+1;

            carry12<=0;

        end

    else if (carry01==1)

        begin

            Q2<=Q2+1;

            carry12<=0;

        end

    end

end

endmodule

```

// Hour //

```

module counter2(Clk, carry01, set, select, SW[7:0], carry12, Q4, Q5);

    input Clk, carry01, carry12, set, select;

    input [7:0] SW;

    output reg [3:0] Q4;

    output reg [3:0] Q5;

    reg en;

    always @(posedge set or posedge carry12)

    begin

        if (carry12==1)

```



```

        en<=0;

    else if (set==1)

        en<=1&select;

    else

        en<=0;

end

always @(posedge Clk)

begin

    if(set)

    begin

        if (Q4==4'd3 & Q5==4'd2 & carry12==1 & carry01==1)

            begin

                Q4<=0;

                Q5<=0;

            end

        else if (Q4==4'd9 & carry12==1 & carry01==1)

            begin

                Q4<=0;

                Q5<=Q5+1;

            end

        else if (Q4==4'd8 & carry12==1 & carry01==1)

            begin

                Q4<=Q4+1;

            end

        else if (carry12==1 & carry01==1)

```

```

begin
    Q4<=Q4+1;
end
else if(en==1)
begin
    Q4<=SW[3:0];
    Q5<=SW[7:4];
end
end
else
begin
    if (Q4==4'd3 & Q5==4'd2 & carry12==1 & carry01==1)
        begin
            Q4<=0;
            Q5<=0;
        end
    else if (Q4==4'd9 & carry12==1 & carry01==1)
        begin
            Q4<=0;
            Q5<=Q5+1;
        end
    else if (Q4==4'd8 & carry12==1 & carry01==1)
        begin
            Q4<=Q4+1;
        end
    else if (carry12==1 & carry01==1)

```

```

        begin

            Q4<=Q4+1;

        end

    end

end

endmodule


// Seven segment display //

module seven_segment(Clk, in, HEX0,set);

    output reg [6:0] HEX0;

    input [3:0] in;

    input Clk,set;

    always @(posedge Clk, posedge set)

    begin

        HEX0[0] <= (~in[3]&~in[2]&~in[1]&in[0])|(in[2]&~in[1]&~in[0])|(in[3]&in[2])|(in[3]&in[1]);

        HEX0[1] <= (in[2]&~in[1]&in[0])|(in[2]&in[1]&~in[0])|(in[3]&in[2])|(in[3]&in[1]);

        HEX0[2] <= (in[3]&in[2])|(in[3]&in[1])|(~in[2]&in[1]&~in[0]);

        HEX0[3] <=
(in[2]&~in[1]&~in[0])|(in[2]&in[1]&in[0])|(in[3]&in[1])|(~in[3]&~in[2]&~in[1]&in[0])|(in[3]&in[2])|(in[3]
&in[0]);

        HEX0[4] <= (in[2]&~in[1])|(in[3]&in[1])|(~in[1]&in[0])|(in[1]&in[0]);

        HEX0[5] <= (in[3]&in[2])|(~in[2]&in[1])|(~in[3]&~in[2]&in[0])|(in[1]&in[0]);

        HEX0[6] <= (~in[3]&~in[2]&~in[1])|(in[3]&in[2])|(in[2]&in[1]&in[0])|(in[3]&in[1]);

    end

endmodule


module seven_segments(Clk, in, HEX0);

```

```

output reg [6:0] HEX0;

input [3:0] in;

input Clk;

always @(posedge Clk)

begin

    HEX0[0] <= (~in[3]&~in[2]&~in[1]&in[0])|(in[2]&~in[1]&~in[0])|(in[3]&in[2])|(in[3]&in[1]);

    HEX0[1] <= (in[2]&~in[1]&in[0])|(in[2]&in[1]&~in[0])|(in[3]&in[2])|(in[3]&in[1]);

    HEX0[2] <= (in[3]&in[2])|(in[3]&in[1])|(~in[2]&in[1]&~in[0]);

    HEX0[3] <=
(in[2]&~in[1]&~in[0])|(in[2]&in[1]&in[0])|(in[3]&in[1])|(~in[3]&~in[2]&~in[1]&in[0])|(in[3]&in[2])|(in[3]
&in[0]);

    HEX0[4] <= (in[2]&~in[1])|(in[3]&in[1])|(~in[1]&in[0])|(in[1]&in[0]);

    HEX0[5] <= (in[3]&in[2])|(~in[2]&in[1])|(~in[3]&~in[2]&in[0])|(in[1]&in[0]);

    HEX0[6] <= (~in[3]&~in[2]&~in[1])|(in[3]&in[2])|(in[2]&in[1]&in[0])|(in[3]&in[1]);

end

endmodule


// Divider //

module div(

output reg o_clk,

input i_clk

);


parameter N=50_000_000;

parameter M=24_999_999;


reg [25:0]cnt;

```

```
always @(posedge i_clk)
```

```
begin
```

```
if(cnt==N-1)
```

```
cnt<=26'b0;
```

```
else
```

```
cnt<=cnt+26'b1;
```

```
end
```

```
always @(posedge i_clk)
```

```
begin
```

```
if(cnt<=M)
```

```
o_clk<=1;
```


```
else
```

```
o_clk<=0;
```


```
end
```

```
endmodule
```

### 3. 實驗結果照片 (optional)

 

#### 4. RTL 佈局(optional)

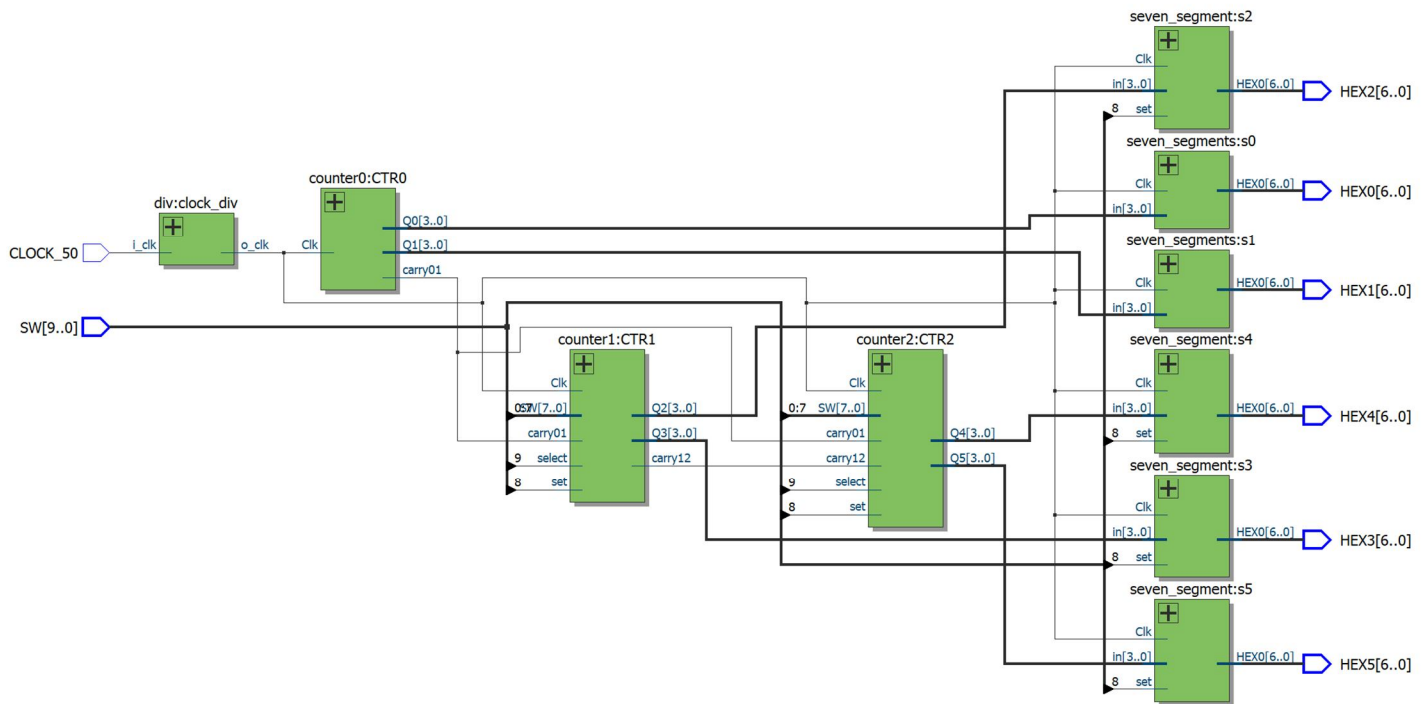

#### 5.問題與討論

本次實驗開始學習如何使用 `always` 語法，不僅從中了解 `Blocking` 和 `Non-blocking` 的差別，並了解到許多硬體描述語法的細節與特別注意的地方，例如：中間節點要宣告為 `wire` 還是 `reg`。另外，本次實驗更學習到 `sequential circuit` 與 `clock` 的實現。